


Digital Logic Design
Computer Assignment 5
Report sheet

Niloufar mortazavi

220701096

نیلوفر مرتضوی

 First we design a sequence detector using moore machine like below:




state table

transition table


state	0	1	w	$v_2 v_1 v_0$	0	1	w
A	B	A	0	000	001	000	0
B	B	C	0	001	001	010	0
C	B	D	0	010	001	011	0
D	B	E	0	011	001	100	0
E	B	F	0	100	001	101	0
F	B	G	0	101	001	110	0
G	H	A	0	110	111	000	0
H	B	C	1	111	001	010	1
state ⁺				$v_2^+ v_1^+ v_0^+$			

 We write the Verilog using the designed states. Then we wrote a testbench and we synthesized the Verilog code using quartus and by writing a testbench to compare pre and post synthesized code we can see the waveform below:







as we can see you can detect some timing differences because we have delays in the synthesized code.

We can access the floor plan:

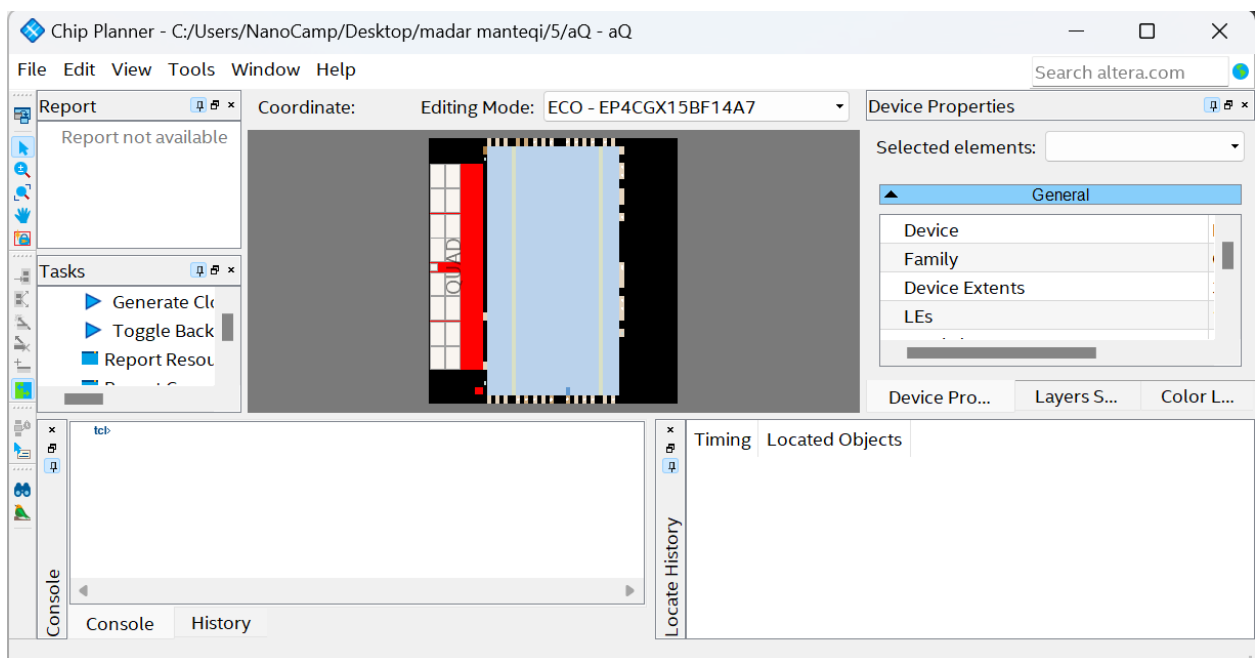


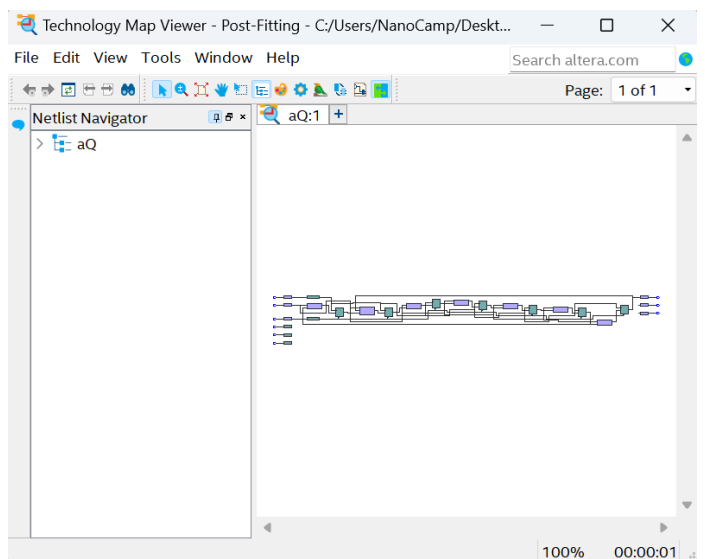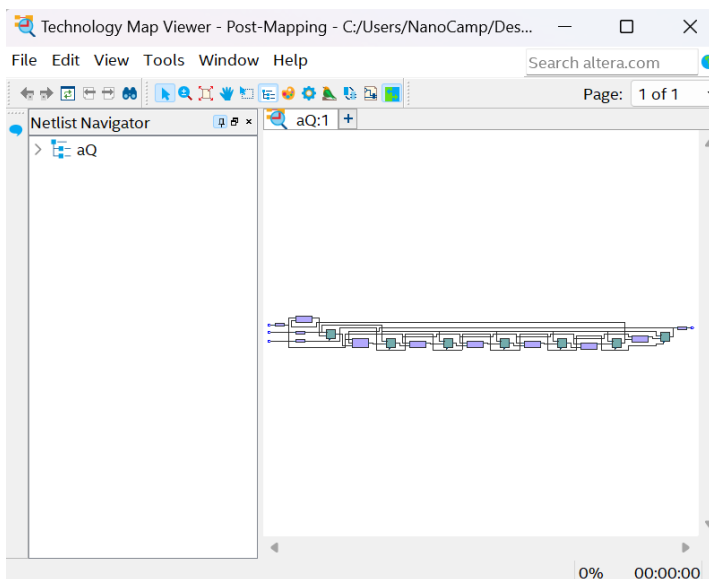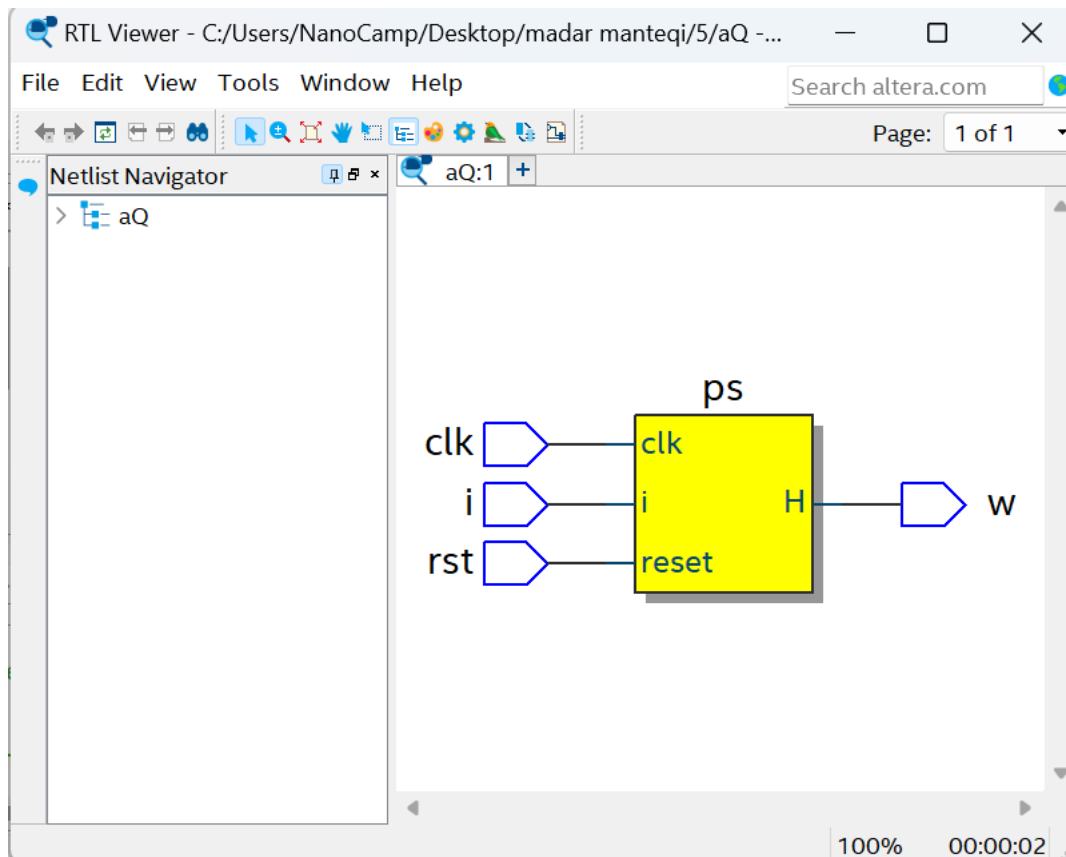
We can see the netlists in netlist viewer:



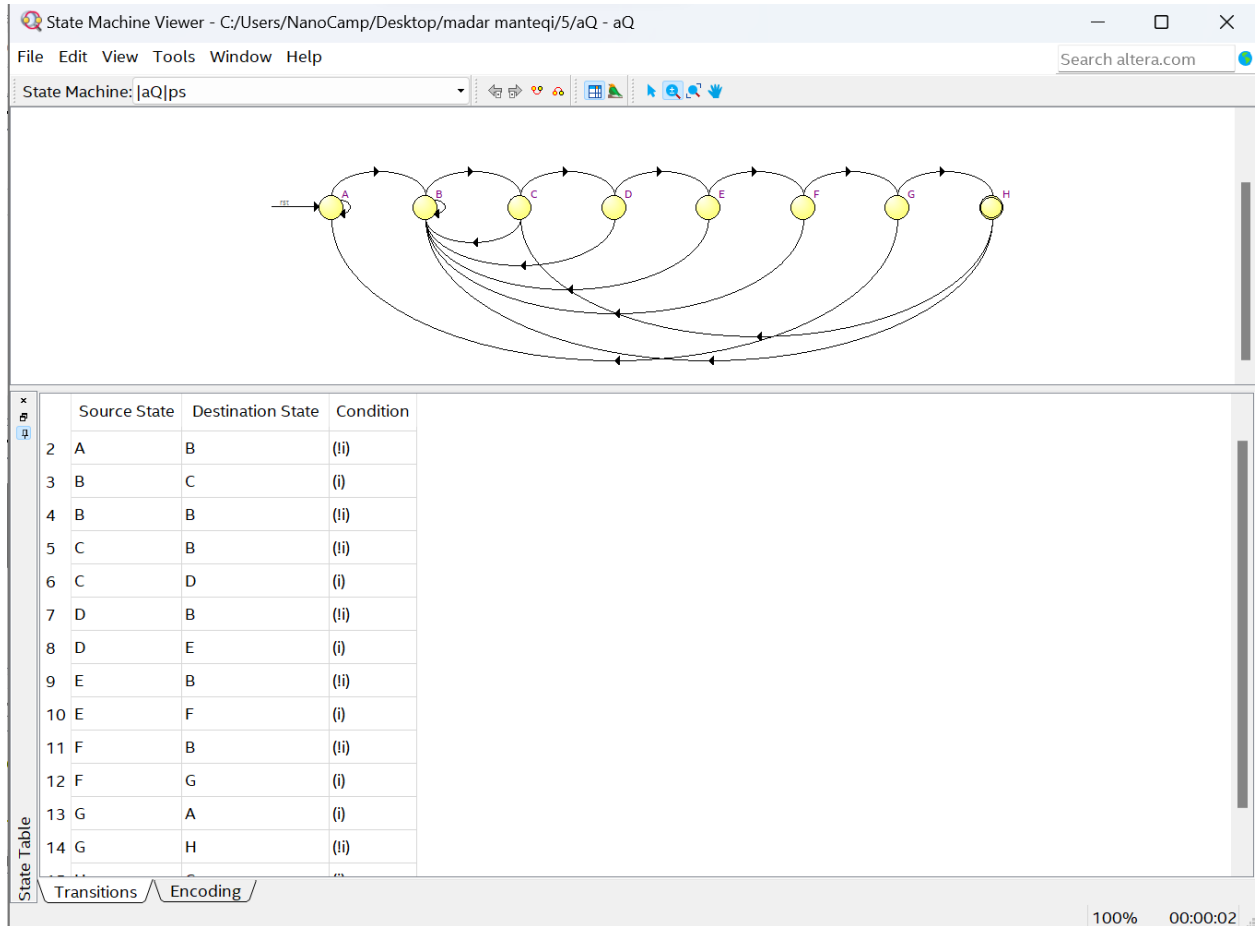

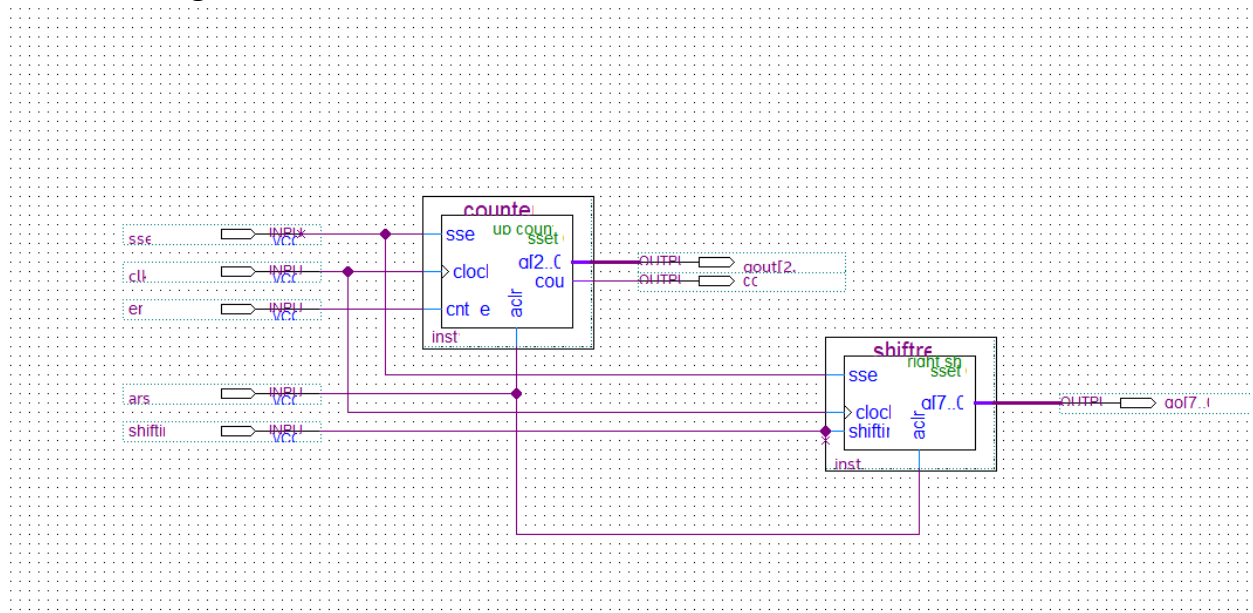For part b we use the Quartus library and by changing the register and the counter we built a reg and bit counter.



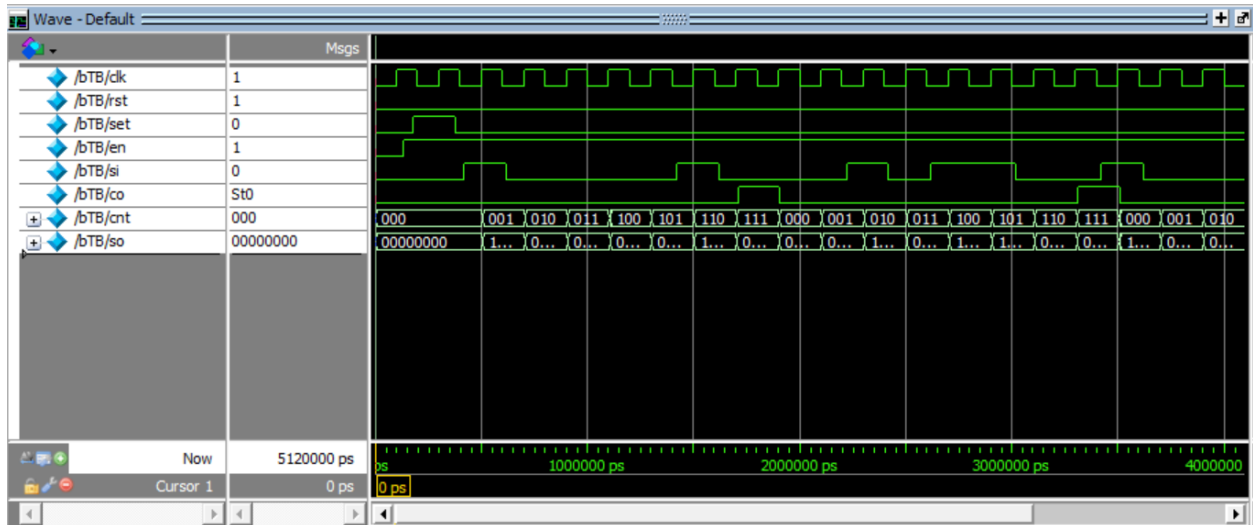

same as the last part we observe the plan floor and the netlist.

